
```
Ayush Goyal
190905522
                         DSD Lab 4 (Week 4)
Q1)
module q41(B,E);
        input [3:0]B;
        output [3:0]E;
        assign E[0] = {}^{\sim}B[0];
        eighttoonemux stage0({1'b0,1'b0,1'b0,1'b1,1'b1,B[0],1'b0,1'b0}, B[3:1], E[3]);
        eighttoonemux stage1({1'b0,1'b0,1'b0,B[0],1'b0,~B[0],1'b1,B[0]}, B[3:1], E[2]);
        eighttoonemux stage2({1'b0,1'b0,1'b0,~B[0],B[0],~B[0],B[0],~B[0]}, B[3:1], E[1]);
endmodule
module eighttoonemux(w,s,f);
        input [7:0]w;
        input [2:0]s;
        output f;
        reg f;
        always @(w or s)
        begin
        case(s)
        0: f = w[0];
        1: f = w[1];
        2: f = w[2];
        3: f = w[3];
        4: f = w[4];
        5: f = w[5];
        6: f = w[6];
        7: f = w[7];
```

endcase

end

## endmodule

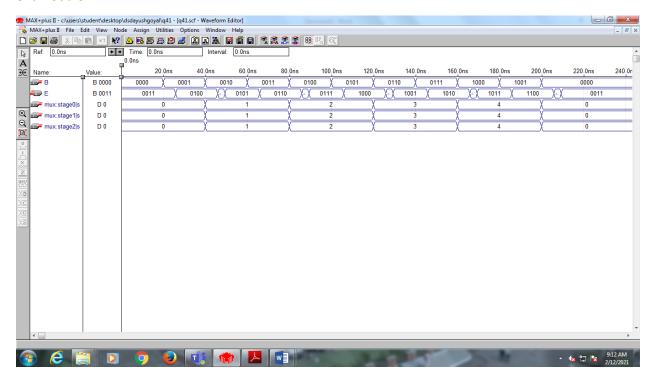


## Q2)

```
module twotofour(a1, en1, f1);
input en1;
input [1:0]a1;
output [3:0]f1;
reg [3:0]f1;
always @(a1 or en1)
begin
case({en1, a1})
3'b000: f1 = 4'b0001;
3'b001: f1 = 4'b0100;
3'b011: f1 = 4'b1000;
```

```
default: f1= 4'b0000;
endcase
end
endmodule

module q22(a, en, f);
input en;
input [3:0]a;
output [15:0]f;
wire [3:0]w;
twotofour first(a[3:2], en, w);
twotofour second(a[1:0], ~w[0], f[3:0]);
twotofour third(a[1:0], ~w[1], f[7:4]);
twotofour fourth(a[1:0], ~w[2], f[11:8]);
twotofour fifth(a[1:0], ~w[3], f[15:12]);
```

## endmodule

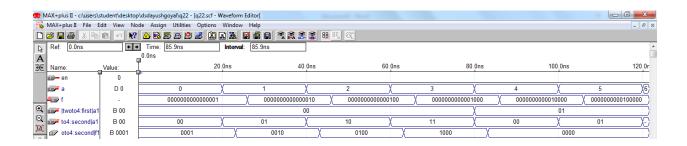



```
Q3)
```

endmodule

